

CECS 440 – Lab 5

ALU and Register File

Due date: 10/16/2025

Name: Eric Santana

ID: 015107467

I certify that this submission is my original work.



Goal

The goal of this lab was to model a CPU datapath in Verilog. The main components were an Arithmetic Logic Unit, a Register File, and an Arithmetic Logic Unit Output Register. Using all these components opens the door to view how a CPU can perform arithmetic and logic operations on values stored in registers.

Steps

1. Opened Vivado and created a new project for ALU and Register File design.
2. Added the design files: alu.v, ALUout.v, regfile.v, and design.v. Imported alu.v from a previous lab.
3. Wrote and completed the Verilog code for each module according to the lab instructions.
4. Created a testbench to simulate the datapath and verify that the outputs matched the expected results for multiple operations.
5. Ran simulation in Vivado, and observed the waveform and console outputs, and confirmed proper functionality for each operation.
6. Verified that each module worked correctly and that the datapath connected to the ALU, Register File, and Output Register as shown in the block diagram.

Results

The ALU and Register File design functioned correctly for all test cases. Each instruction performed the correct arithmetic or logic operation based on the opcode, and the results were stored properly in the ALU output register. The simulation console and waveform confirmed the expected behavior for the operations.

Conclusion

This lab helped reinforce the concept of how a CPU can perform instructions on values stored in different registers. It showed me how data is read from a register and processed through the CPU's ALU and written back to store the result of an arithmetic or logic operation.

Appendix (1 out of 2)

Waveforms



Appendix (2 out of 3)

Console Output

```
Checking test case
srca =          500, srcb =          1000
add $ALUout, $ 3, $ 4 performed
sum =          1500
test passed

Checking test case
srca =          500, srcb =          1000
increment $ALUout, $ 3 performed
d_out =          501
test passed

Checking test case
srca = ffff0000, srcb = 0a0a0a0a
and $ALUout, $ 1, $ 2 performed
d_out = 0a0a0000
test passed

Checking test case
srca = ffff0000, srcb = 0a0a0a0a
or $ALUout, $ 1, $ 2 performed
d_out = ffff0a0a
test passed

Checking test case
srca = 0a0a0a0a, srcb = ffff0000
xor $ALUout, $ 2, $ 1 performed
d_out = f5f50a0a
test passed

Checking test case
srca = 0a0a0a0a, srcb = ffff0000
not $ALUout, $ 2 performed
d_out = f5f5f5f5
test passed


Checking test case
srca =          1000, srcb = 4294901760
sll $ALUout, $ 4, performed
d_out =          2000
test passed

Checking test case
srca = 000003e8, srcb = ffff0000
nop operation performed
d_out = 00000000
test passed
$finish called at time : 146 ns : File "C:/U
INFO: [USF-XSim-96] XSim completed. Design s
```

Appendix (3 out of 3)

Code

ALUout.v

 

```
//Class: CECS 440
//Lab: 5
//Name: Eric Santana
//ID: 015107467

module ALUout #(parameter width = 8)
    (input clk, reset, load,
     input [width - 1:0] d,
     output reg [width - 1:0] q);

    always @(posedge clk)
    begin
        if(reset) q <= {width{1'b0}};
        else if(load) q <= d;
    end
endmodule
```

Design.v

```
//Class: CECS 440
//Lab: 5
//Name: Eric Santana
//ID: 015107467

`include "regfile.v"
`include "ALUout.v"
`include "alu.v"

`define datasize 32

module simple_datapath
    (input [2:0] op_code,
     input clk, reset,
     input [4:0] rs, rt, rd,
     input wr_en,
     input [`datasize - 1:0] d_in,
     output [`datasize - 1:0] d_out,
     output c, n, z, p);

    wire [`datasize - 1:0] srca, srcb, aluout, aluout_y; // rfDataOut1, rfDataOut2

    regfile #(`datasize) rf
        (.clk(clk),
         .wr_en(wr_en),
         .rd_addr1(rs),
         .rd_addr2(rt),
         .wr_addr(rd),
         .wr_data(d_in),
         .rd_data1(srca),
         .rd_data2(srcb)
        ); // fill in the port list

    alu #(`datasize) al
        (.a(srca),
         .b(srcb),
         .aluop(op_code),
         .y(aluout_y),
         .c(c),
         .n(n),
         .z(z),
         .p(p)
        ); // fill in the port list

    ALUout #(`datasize) ALUout
        (.clk(clk),
         .reset(reset),
         .load(1'b1),
         .d(aluout_y),
         .q(aluout)
        );

    assign d_out = aluout;
endmodule
```

Alu.v

```
1  timescale 1ns / 1ps
2  //Class: CECS 440
3  //Lab: 5
4  //Name: Eric Santana
5  //ID: 015107467
6
7
8  module alu # (parameter width = 8)
9  (
10     input [width-1:0] a,b,
11     input [2:0] aluop,
12     output reg [width-1:0] y,
13     output reg c, n, z, p
14 );
15
16 always @ (a, b, aluop)
17 begin
18     {y,c,n,z,p} = 0;
19     case(aluop)
20     0: {c,y} = a +b;
21     1:{c,y} = a + 1;
22     2:y = a&b;
23     3:y = a|b;
24     4:y = a^b;
25     5:y = ~a;
26     6:{c,y} = a <<1;
27     7:y = 0;
28     default: y = 32'bz;
29     endcase
30
31     n = y[width-1];
32     z = !y;
33     p = ^y;
34 end
35
36 endmodule
37
```

Regfile.v

```
1 //Class: CECS 440
2 //Lab: 5
3 //Name: Eric Santana
4 //ID: 015107467
5
6
7 module regfile #(parameter width = 8)
8     (input clk,
9      input wr_en, // write enable
10     input [4:0] rd_addr1, rd_addr2, wr_addr, // rs, rt, rd
11     input [width - 1:0] wr_data, // d_in = data in
12     output [width - 1:0] rd_data1, rd_data2); // srca, srcb
13
14     reg [31:0] rf[31:0];
15
16
17     always @(negedge clk)
18         if (wr_en) rf[wr_addr] <= wr_data;
19
20     assign rd_data1 = (rd_addr1 != 5'd0) ? rf[rd_addr1][width-1:0]:{width{1'b0}};
21     assign rd_data2 = (rd_addr2 != 5'd0) ? rf[rd_addr2][width-1:0]:{width{1'b0}};
22
23 endmodule
24
```


testbench

```
1 //Class: CECS 440
2 //Lab: 5
3 //Name: Eric Santana
4 //ID: 015107467
5
6
7 module datapathTester();
8     reg [2:0] op_code;
9     reg clk, reset;
10    reg [4:0] rs, rt, rd;
11    reg wr_en;
12    reg [31:0] d_in;
13    wire [31:0] d_out;
14    wire c,n,z,p;
15
16    integer i;
17
18    simple_datapath dut
19        (.op_code(op_code),
20         .clk(clk),
21         .reset(reset),
22         .rs(rs),
23         .rt(rt),
24         .rd(rd),
25         .wr_en(wr_en),
26         .d_in(d_in),
27         .d_out(d_out),
28         .c(c),
29         .n(n),
30         .z(z),
31         .p(p)
32        );
33
34
35    always #5 clk = ~clk;
36
37    initial begin
38        op_code = 0;
39        clk = 0;
40        {rs, rt, rd} = 0;
41        wr_en = 0;
42        d_in = 0;
43
44        reset = 0;
45        #10;
46        reset = 1;
47        #10;
48        reset = 0;
49        #10;
50
51        //load registers with values
52        dut.rf.rf[0] = 0;
53        dut.rf.rf[1] = 32'hFFFF0000;
54        dut.rf.rf[2] = 32'h0A0A0A0A;
55        dut.rf.rf[3] = 32'd500;
56        dut.rf.rf[4] = 32'd1000;
57        //load remaining registers with random values
```

```

)   for(i = 5; i < 32; i = i + 1)
)       begin
)           dut.rf.rf[i] = i;
)       end

)   $display("Registers Initialized!");
)   showRegisterContents();
)   //perform ALU operations
)   //Test case 1: add $ALUout, $3, $4
)       @(negedge clk)
)           op_code = 3'b000;
)           rs = 5'b00011; // 3
)           rt = 5'b00100; // 4
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 2: inc $ALUout, $3
)       @(negedge clk)
)           op_code = 3'b001;
)           rs = 5'b00011; // 3
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 3: and $ALUout, $1, $2
)       @(negedge clk)
)           op_code = 3'b010;
)           rs = 5'b00001; // 1
)           rt = 5'b00010; // 2
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 4: or $ALUout, $1, $2
)       @(negedge clk)
)           op_code = 3'b011;
)           rs = 5'b00001; // 1
)           rt = 5'b00010; // 2
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 5: xor $ALUout, $2, $1
)       @(negedge clk)
)           op_code = 3'b100;
)           rs = 5'b00010; // 2
)           rt = 5'b00001; // 1
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 6: not $ALUout, $2
)       @(negedge clk)
)           op_code = 3'b101;
)           rs = 5'b00010; // 2
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 7: sl $ALUout, $4
)       @(negedge clk)
)           op_code = 3'b110;
)           rs = 5'b00100; // 4
)       @(posedge clk) #1
)           checkOperation();
)       //Test case 8: nop
)       @(negedge clk)
)           op_code = 3'b111;

```

```

118
119
120 $finish;
121
122
123 end
124
125 task showRegisterContents;
126 //look directly into the register file to see contents
127 begin
128     $display("\tRegister\tContent");
129     for(i = 0; i < 32; i = i + 1)
130     begin
131         #1 $display("%d\t0x%h", i, dut.rf.rf[i]);
132     end
133 end
134 endtask //end of showRegisterContents task
135
136 task checkOperation;
137 begin
138     $display("\nChecking test case");
139     if(op_code == 0 || op_code == 1 || op_code == 6)
140         //display arithmetic operation values in decimal
141         $display("srca = %d, srcb = %d",dut.srca, dut.srcb);
142     else
143         //display logical operation values in hex
144         $display("srca = %h, srcb = %h",dut.srca, dut.srcb);
145
146     case(op_code)
147     0: begin
148         $display("add $ALUout, $%d, $%d performed",rs,rt);
149         $display("sum = %d",d_out);
150         if(d_out == (dut.rf.rf[rs]+dut.rf.rf[rt])) begin
151             $display("test passed");
152         end
153         else begin
154             $display("Test Failed!!!");
155         end
156     end
157     1: begin
158         $display("increment $ALUout, $%d performed",rs);
159         $display("d_out = %d",d_out);
160         if(d_out == (dut.rf.rf[rs]+1))
161             $display("test passed");
162         else begin
163             $display("Test Failed!!!");
164         end
165     end
166     2: begin
167         $display("and $ALUout, $%d, $%d performed",rs,rt);
168         $display("d_out = %h",d_out);
169         if(d_out == (dut.rf.rf[rs]&dut.rf.rf[rt]))
170             $display("test passed");
171         else
172             $display("Test Failed!!!");
173     end
174     3: begin

```

```

159 ○ $display("d_out = %d",d_out);
160 ○ if(d_out == (dut.rf.rf[rs]+1))
161 ○     $display("test passed");
162 ○ else begin
163 ○     $display("Test Failed!!!");
164 ○ end
165 end
166 2: begin
167 ○     $display("and $ALUout, %d, %d performed",rs,rt);
168 ○     $display("d_out = %h",d_out);
169 ○     if(d_out == (dut.rf.rf[rs]&dut.rf.rf[rt]))
170 ○         $display("test passed");
171 ○     else
172 ○         $display("Test Failed!!!");
173 ○ end
174 3: begin
175 ○     $display("or $ALUout, %d, %d performed",rs,rt);
176 ○     $display("d_out = %h",d_out);
177 ○     if(d_out == (dut.rf.rf[rs]|dut.rf.rf[rt]))
178 ○         $display("test passed");
179 ○     else
180 ○         $display("Test Failed!!!");
181 ○ end
182 4: begin
183 ○     $display("xor $ALUout, %d, %d performed",rs,rt);
184 ○     $display("d_out = %h",d_out);
185 ○     if(d_out == (dut.rf.rf[rs]^dut.rf.rf[rt]))
186 ○         $display("test passed");
187 ○     else
188 ○         $display("Test Failed!!!");
189 ○ end
190 ○ 5: begin    $display("not $ALUout, %d performed",rs);
191 ○     $display("d_out = %h",d_out);
192 ○     if(d_out == (~dut.rf.rf[rs]))
193 ○         $display("test passed");
194 ○     else
195 ○         $display("Test Failed!!!");
196 ○     end
197 ○ 6: begin    $display("sll $ALUout, %d, performed",rs);
198 ○     $display("d_out = %d",d_out);
199 ○     if(d_out == (dut.rf.rf[rs]*2))
200 ○         $display("test passed");
201 ○     else
202 ○         $display("Test Failed!!!");
203 ○     end
204 ○ 7: begin    $display("nop operation performed");
205 ○     $display("d_out = %h",d_out);
206 ○     if(!d_out)
207 ○         $display("test passed");
208 ○     else
209 ○         $display("Test Failed!!!");
210 ○     end
211 ○     default: $display("ERROR: Invalid Operation!");
212 endcase
213 end
214 endtask    //end of checkOperation task
215 endmodule

```

Use of AI Tools:

ChatGPT Edu (GPT-5) was used to proofread the lab report for clarity and formatting.